

ADC → Analog to Digital Convert

↳ ① Volt

$$3.3V \longrightarrow 1011100$$


↳ ② Common Use Sensor

ADC

↳ No. of Bits (Resolution)

↳ Reference → $\frac{\text{volt}}{\text{Max volt}}$

↳ Circuit → to convert

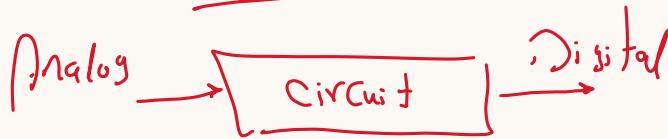

↳ Resolution → 2

↳ Volt Reference → V Ref


↳ Digital Volt = 11 →

ADC ⇒ Max Volt - step

$$\text{step} = \frac{\text{Max Volt}}{2^{\text{Res}}} = \frac{V_{\text{Ref}}}{2^{\text{Res}}} = \frac{4}{2^2} = 1V$$

00	→ 0V
01	→ step × 0 + step × 1 = 1V
10	→ step × 2 + step × 0 = 2V
(11)	→ step × 2 + step × 1 = 3V

DAC → Digital to Analog.

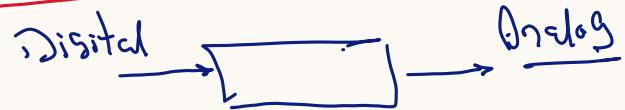

↳ No. of Bits

↳ V Ref


↳ step

$$\text{Analog Volt} = \text{Digital} \times \underline{\text{step}}$$

$$= 0110 \ 0110 * \frac{V_{\text{ref}}}{2^{\text{Res}}}$$

* Atmega32 → port 5, port 7
DAC

ADC . Circuit

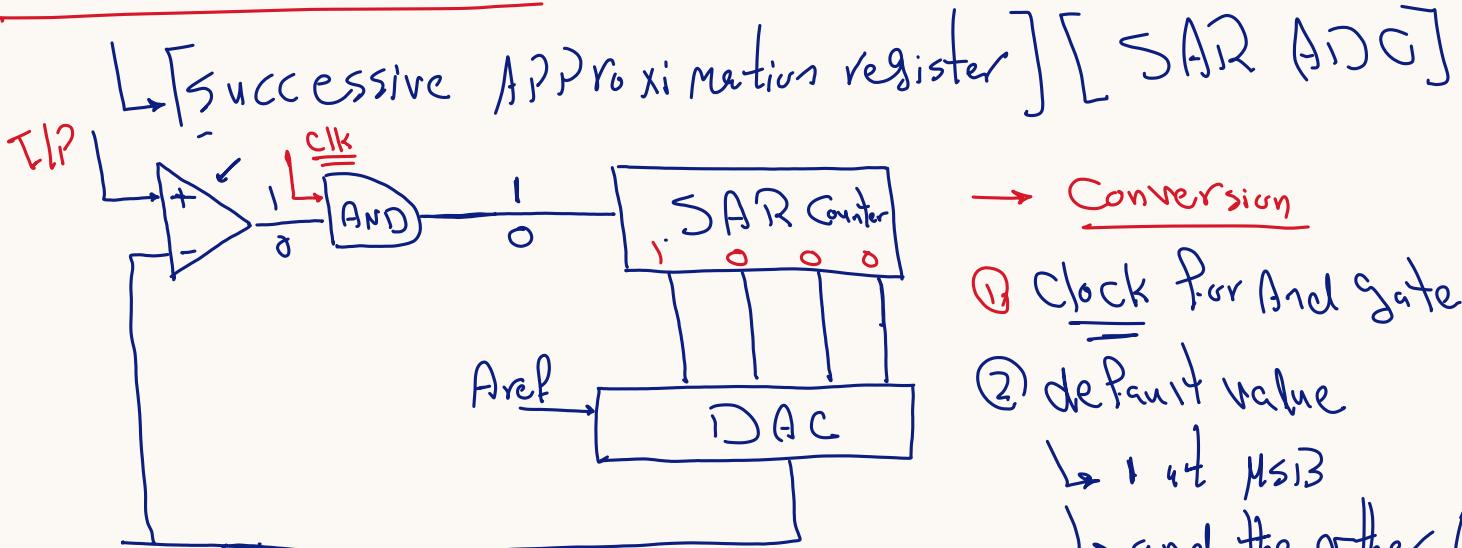

→ Conversion

① Clock for And gate.

② default value

↳ 1 at MSB


↳ and the other bit

③ DAC Convert to Analog

④ Compare

$$\boxed{1} \text{ Aref} = 5V \quad \boxed{2} \text{ Resolution} = 4$$
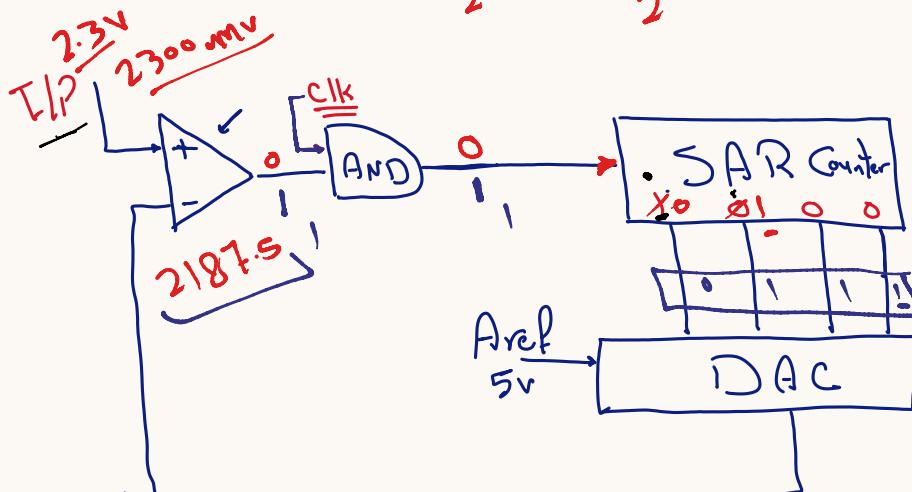
$$\boxed{3} \text{ Step} = \frac{5V}{2^4} = \frac{5000}{2^4} : 312.5 \text{ mV}$$



$$\boxed{4} \text{ SAR Counter} = 1000$$

$$\begin{aligned} \boxed{5} \text{ DAC} &\rightarrow \\ \text{Analog} &= \text{Digital} \times \text{Step} \\ &= 8 \times 312.5 \text{ mV} \\ &= 2500 \text{ mV} \end{aligned}$$

$\boxed{6}$ OP AMP

IP < Feed Back

2300 mV < 2500 mV

* → $\overline{Q_1}$

$\boxed{7}$ AND gate

Clock → 1
OP AMP → 0 → $\overline{Q_1}$

$\boxed{8}$ SAR → Input for SAR Counter = 0

when Input SAR = 0

↳ last Bit will be zero

↳ next Bit will be one

$\boxed{0100} \rightarrow$ New Value for SAR

6) DAC \rightarrow $\frac{0100}{4} * 312.5 \Rightarrow 1250 \text{ mV}$

7) OPAMP \rightarrow IP > Feed Back
 $2300 > 1250 \rightarrow \text{H}$

8) And \rightarrow OPAMP $\rightarrow 1$
Clk $\rightarrow 1$ $\rightarrow \text{H}$

9) SAR \rightarrow Input H

if Input = 1

↳ the last bit still the same value
↳ the next bit will be one

0 110 \rightarrow

10) DAC $\rightarrow 6 * 312.5 \Rightarrow 1875 \text{ mV}$

11) OPAMP $\rightarrow 2300 > 1875 \rightarrow \text{H}$

12) AND \rightarrow OP $\rightarrow 1$
Clk $\rightarrow 1$ $\rightarrow 1$

13) SAR $\rightarrow \text{H}$
0 111 $\rightarrow \text{H} \rightarrow$

14) DAC $\rightarrow 7 * 312.5 \Rightarrow 2187.5 \text{ mV} \rightarrow \boxed{0111}$


ADC in ATmega32

* Conversion time \rightarrow depend on ADC clock

* 15 Kilo sample per second \rightarrow 15 Kilo conversion
in one second.


→ Single Ended & Differential

Single Ended

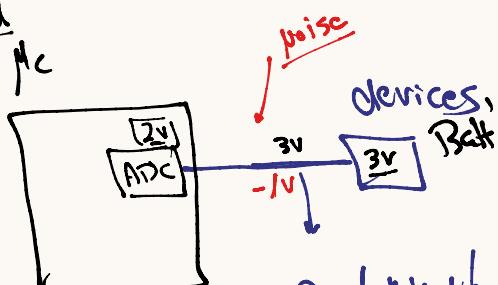


sent the analog voltage b/t one wire

Differential

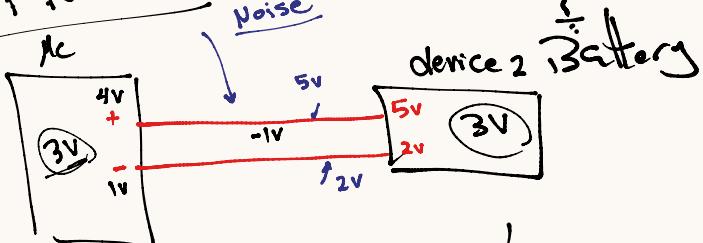


sent the 2 value b/t two wires → and MC will differential this two

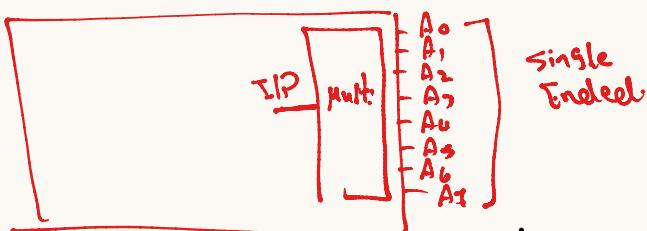↳ 8 multiplexed Single Ended Input channels.



↳ 7, 8: Differential Input channel

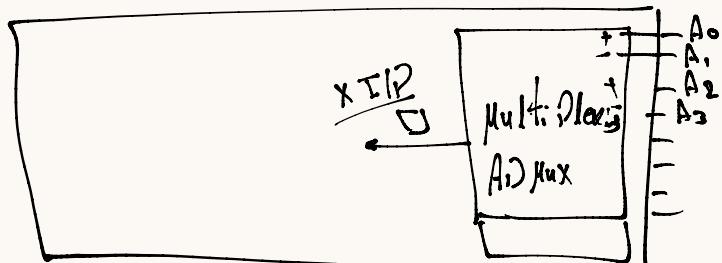


↳ 2 Differential TIP Channel with gain → $\frac{1}{200}$

$$\frac{1000}{2^10} = \frac{1000}{1024} \approx 0.976 \text{ mV}$$

$$\frac{1}{200} = 0.5 \text{ mV}$$

)

ADC Register

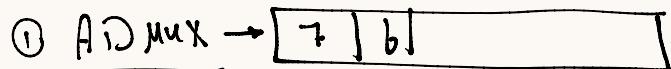

* Bit 7:b :: Reference Selection

① Connect on Aref Pin External Volt (0,0)



② Connect Aref with AVcc (0,1)

③ Reserved (1,0) Not used.

④ Internal Voltage 2.56V →




Bit 5 → left Adjust Result.

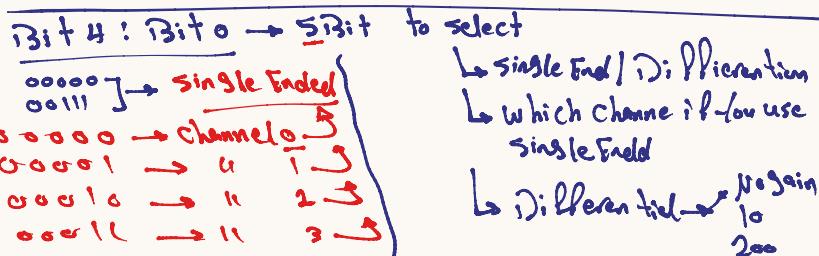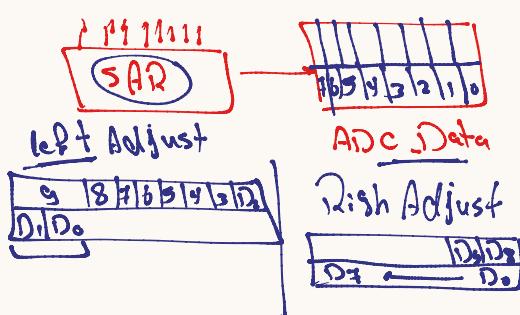

Differential → 1 gain

10000
11101

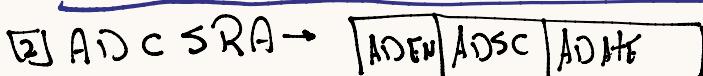

* Bit 7 → ADC_Enable

Not have power
↳ 1 → Enable
↳ 0 → turn off

Bit 6: ADC_Start Conversion


↳ have start conversion operation from Analog to digital.

Single Conversion Mode

→ T1 → b/s/w → start conv
→ T0 → b/H.w → Conv. finished

Free Running Mode (Auto trigger)

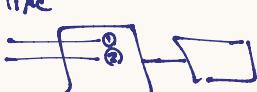
↳ start conversion
↳ must be one at first time



Notes: ① Must enable ADC first


② must set this bit each time

ADC SRA

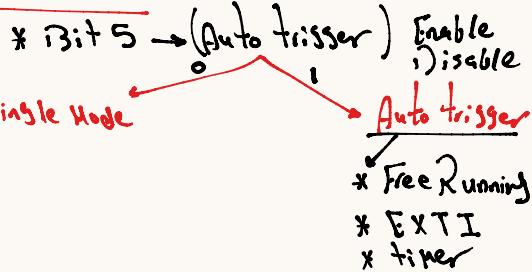

Bit 4: ADC Interrupt Flag

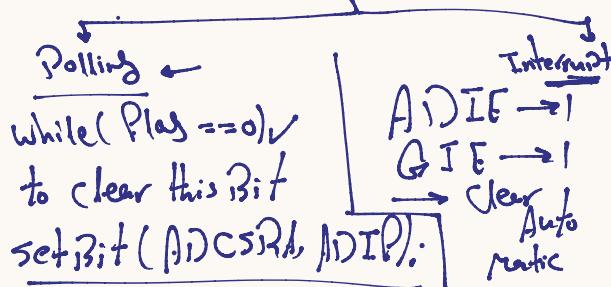* this flag will be set when conversion finish & data store in register



Bit 3 → ADC Interrupt Enable

↳ SIE

↳ 0 → not allow ADC interrupt proc


↳ 1 → allow ADC interrupt proc

but must GIE = 1

ADC Interrupt No → 1b

void __vector_1b() __attribute__()

Bit 2:0 ↳ Prescaler to select ADC_Clock

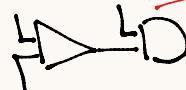

→ system clock / Division Factor
8000 000 1 2 = 4 MHz
4 = 1 MHz

③ Data Register

ADC H ↳ store the digital volt
ADC L

#define ADC_H *(volatile uint8_t *) 0x25

#define ADC_L *(volatile uint8_t *) 0x26

#define ADC_D *(volatile uint16_t *) 0x27

ADC_D → [0x24]
[0x25]



